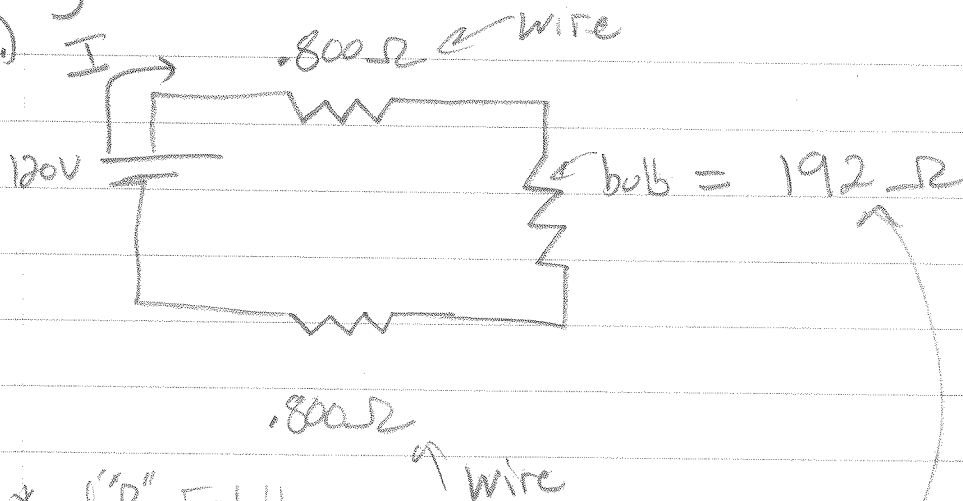


Pg 578 #3

3.)



*need "R" for bulb

$$P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P} = \frac{(120V)^2}{75W} = 192\ \Omega$$


* Since wires have some resistance, the bulb does not actually receive 120V of energy, so the wattage of the bulb would be lower than 75W

↳ need to determine "I" for circuit


$$I = \frac{\Delta V}{R_{eq}} = \frac{120V}{(.800\ \Omega + 192\ \Omega + .800\ \Omega)} = .62\ \text{amps}$$

$$P = I^2 R \rightarrow P = (.62\ \text{amps})^2 (192\ \Omega) = 73.8\ \text{watts}$$

Pg 578:6 & 7 (Find voltage drop & power for each resistor) 14
65

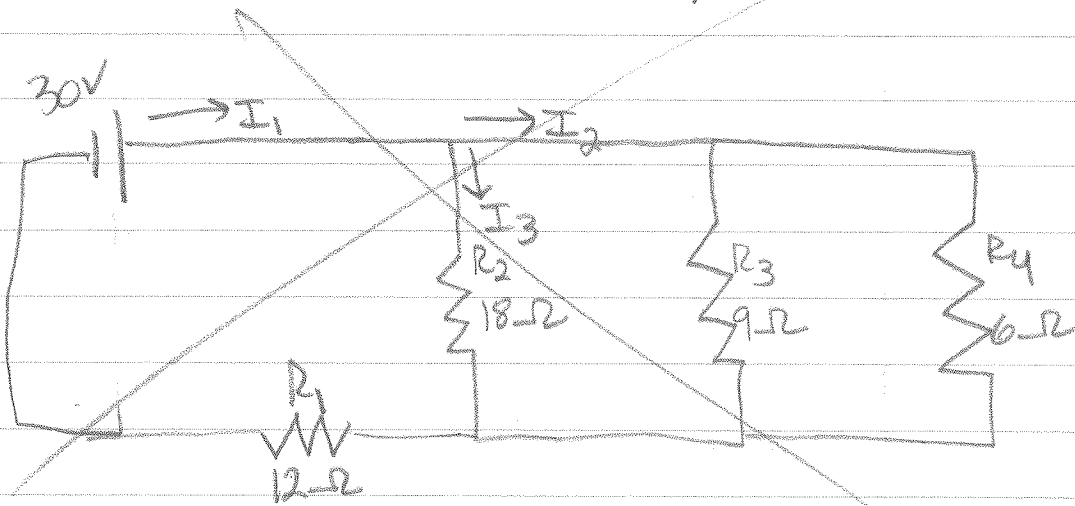

Pg 578: 4
4 a)

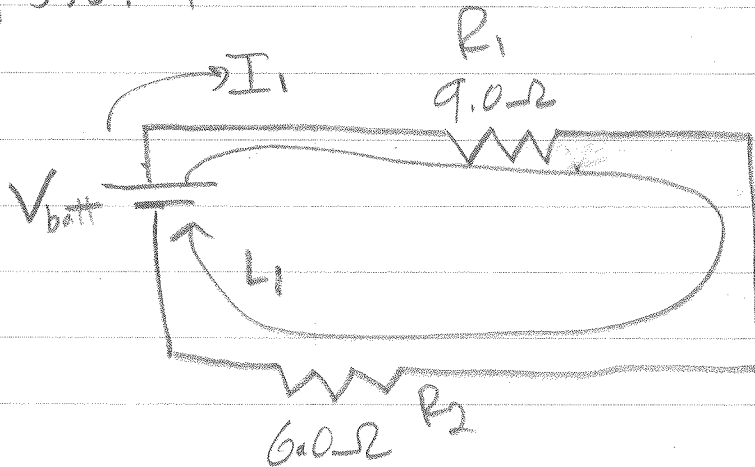

* I_1 is equal @ all points in circuit, so we can use the 6.0Ω resistor & its voltage drop to determine I_1

$$V_{6.0\Omega} = I_1 \cdot R_{6.0\Omega} \rightarrow I_1 = \frac{V_{6.0\Omega}}{R_{6.0\Omega}} = \frac{12V}{6.0\Omega} = 2 \text{ amps}$$

Loop Eq for L_1 can now determine V_{batt}

$$L_1 \rightarrow \Delta V = 0V = V_{batt} - V_{9.0\Omega} - V_{6.0\Omega}$$

$$\hookrightarrow \Delta V = 0V = V_{batt} - I_1 \cdot R_1 - I_1 \cdot R_2$$

$$\hookrightarrow \Delta V = 0V = V_{batt} - (2 \text{ amps} \cdot 9.0\Omega) - (2 \text{ amps} \cdot 6.0\Omega)$$

$$V_{batt} = 30V$$

Power In Each Resistor $P = IV = \frac{V^2}{R} = I^2 \cdot R$


- For 9.0Ω

$$\hookrightarrow P = I^2 \cdot R = (2 \text{ amps})^2 \cdot 9.0\Omega = 36 \text{ Watts}$$

- For 6.0Ω

$$\hookrightarrow P = I^2 \cdot R = (2 \text{ amps})^2 \cdot 6.0\Omega = 24 \text{ Watts}$$

Pg 578 #4b

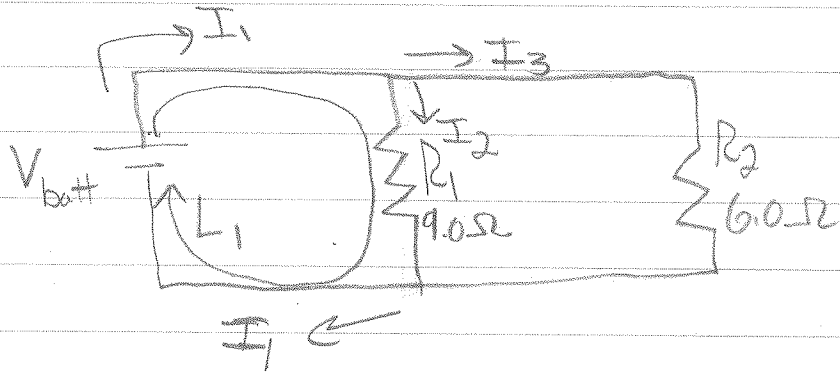

$$I_2 = .25 \text{ amps}$$

$$\Delta V_{L_1} = 0 \text{ V} = V_{\text{batt}} - V_{R_1} = V_{\text{batt}} - I_2 \cdot R_1$$


$$\rightarrow V_{\text{batt}} = I_2 \cdot R_1 = .25 \text{ amps} \cdot 9.0 \Omega \quad V_{\text{batt}} = 2.3 \text{ V}$$

To determine Power in Each Resistor


$$R_1 \rightarrow P = I^2 R = (I_2)^2 \cdot R_1 = (.25 \text{ amps})^2 (9.0 \Omega) = .563 \text{ watts}$$

$$R_2 \rightarrow P = \frac{V^2}{R} = \frac{(2.3 \text{ V})^2}{(6.0 \Omega)} = .882 \text{ watts}$$

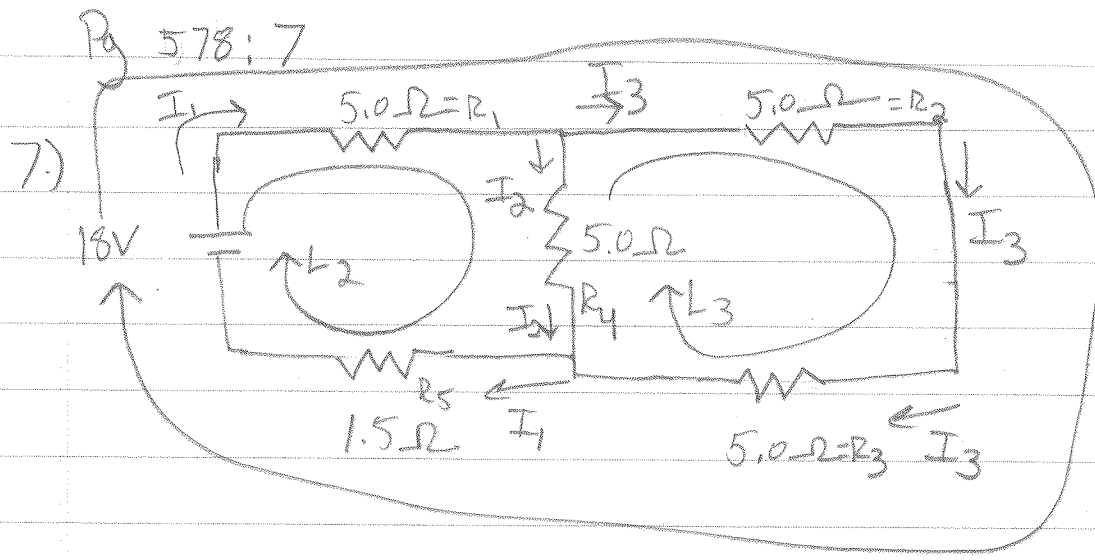* Voltage for resistors in parallel is all same, and same as battery (2.3 V)




L_1 redrawn

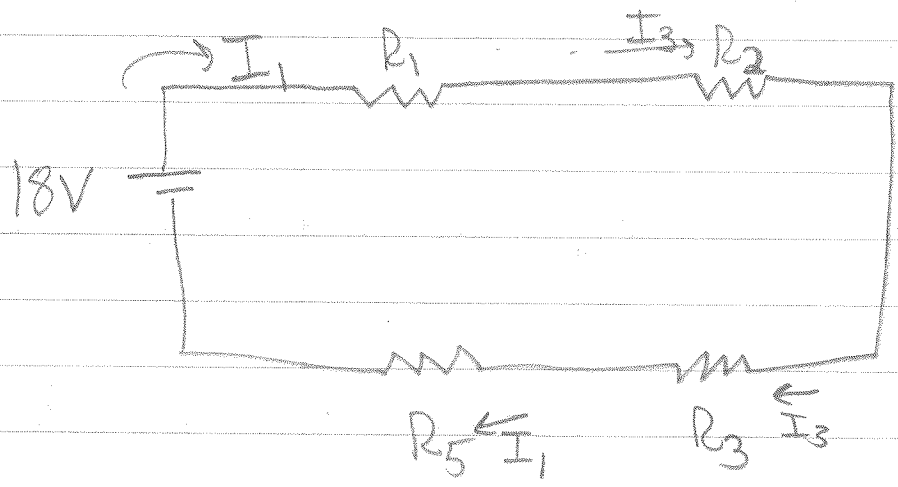


$L_1 \Delta V = 0V = 18V - V_{R1} - V_{R2} - V_{R3} - V_{R5}$
 $0V = 18V - I_1 R_1 - I_3 R_2 - I_3 R_3 - I_1 R_5$

L_2 redrawn


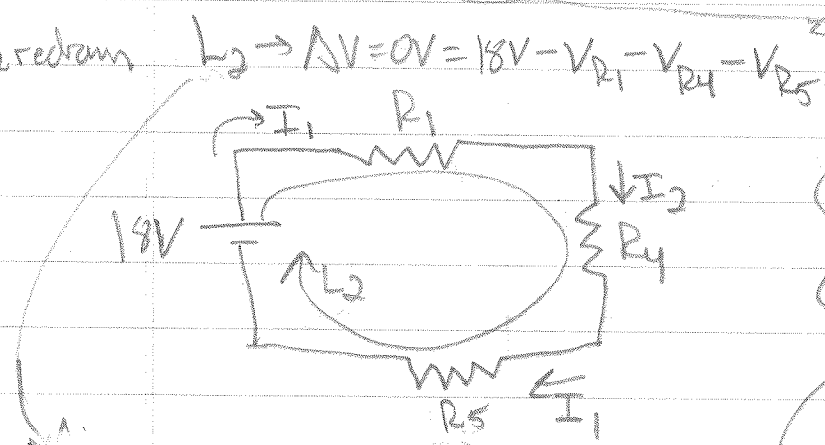


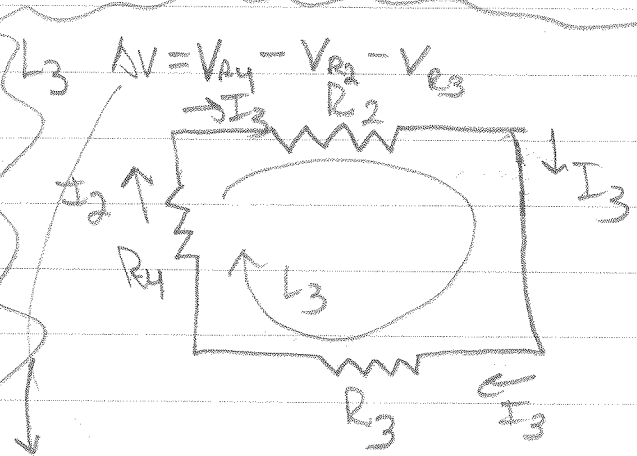$\Delta V = 0V = 18V - I_1 R_1 - I_2 R_4 - I_1 R_5$




$\Delta V = 0V = I_2 R_4 - I_3 R_2 - I_3 R_3$


14)

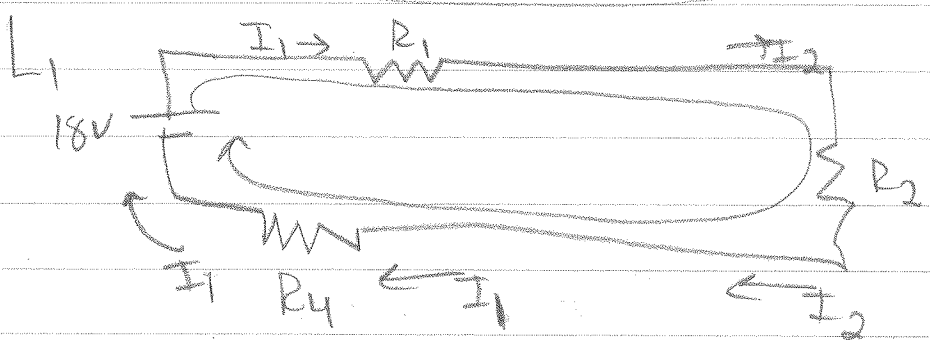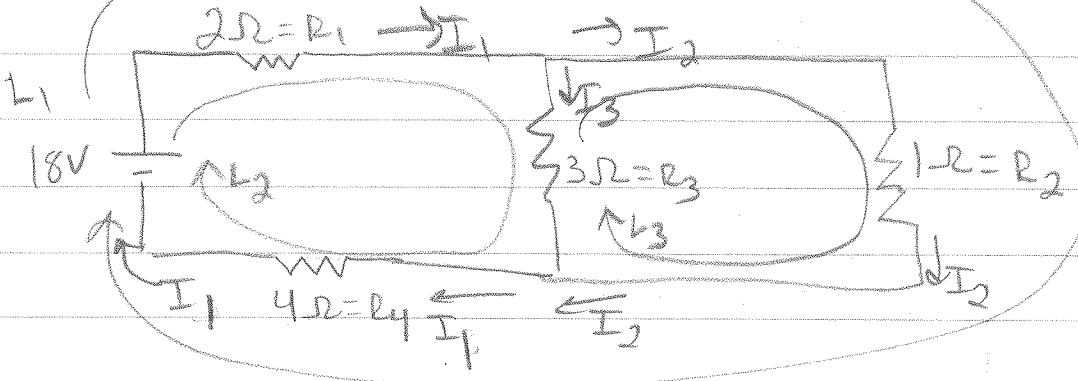

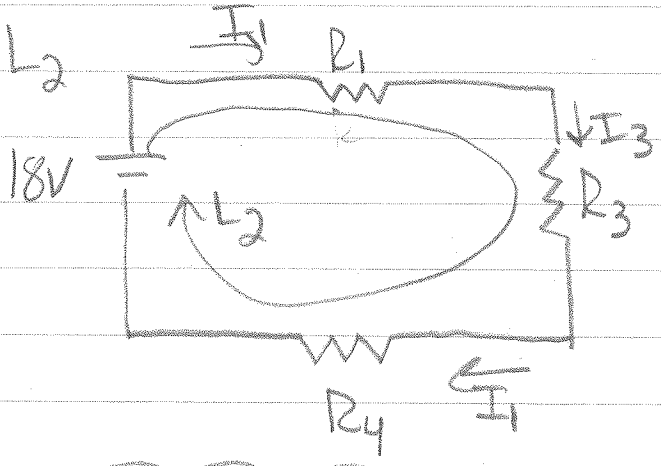$\Delta V = 0V = 18V - V_{R1} - V_{R2} - V_{R4} = 18V - I_1 R_1 - I_2 R_2 - I_1 R_4$



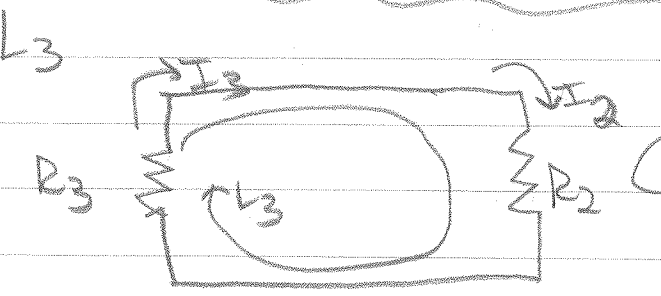$\Delta V = 0V = 18V - V_{R1} - V_{R3} - V_{R4}$
 $\Delta V = 0V = 18V - I_1 R_1 - I_3 R_3 - I_1 R_4$



$\Delta V = 0V = V_{R3} - V_{R2}$
 $\Delta V = 0V = I_3 R_3 - I_2 R_2$