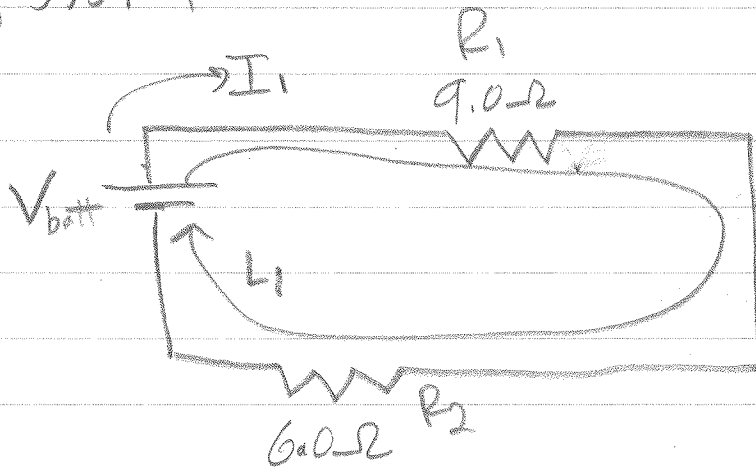


Pg 578: 4  
4 a)



\*  $I_1$  is equal @ all points in circuit, so we can use the  $6.0 \Omega$  resistor & its voltage drop to determine  $I_1$

$$\begin{aligned} \rightarrow V_{6.0\Omega} &= I_1 \cdot R_{6.0\Omega} \rightarrow I_1 = \frac{V_{6.0\Omega}}{R_{6.0\Omega}} = \frac{12V}{6.0\Omega} = 2 \text{ amps} \end{aligned}$$

Loop Eq for  $L_1$  can now determine  $V_{batt}$

$$L_1 \rightarrow \Delta V = 0V = V_{batt} - V_{9.0\Omega} - V_{6.0\Omega}$$

$$\rightarrow \Delta V = 0V = V_{batt} - I_1 \cdot R_1 - I_1 \cdot R_2$$

$$\rightarrow \Delta V = 0V = V_{batt} - (2 \text{ amps} \cdot 9.0\Omega) - (2 \text{ amps} \cdot 6.0\Omega)$$

$$\underline{V_{batt} = 30V}$$

Power In Each Resistor  $P = IV = \frac{V^2}{R} = I^2 \cdot R$


- For  $9.0 \Omega$

$$\rightarrow P = I^2 \cdot R = (2 \text{ amps})^2 \cdot 9.0\Omega = 36 \text{ Watts}$$

- For  $6.0 \Omega$

$$\rightarrow P = I^2 \cdot R = (2 \text{ amps})^2 \cdot 6.0\Omega = 24 \text{ Watts}$$

Pg 578 #4b

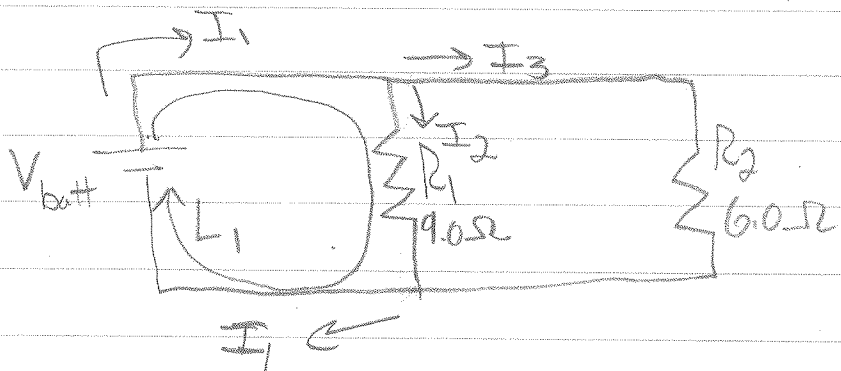

$$I_2 = .25 \text{ amps}$$

$$\Delta V_{L_1} = 0V = V_{\text{batt}} - V_{R_1} = V_{\text{batt}} - I_2 \cdot R_1$$

$$\rightarrow V_{\text{batt}} = I_2 \cdot R_1 = .25 \text{ amps} \cdot 9.0 \Omega \quad V_{\text{batt}} = 2.3 \text{ V}$$

To determine Power in Each Resistor

$$R_1 \rightarrow P = I^2 R = (I_2)^2 \cdot R_1 = (.25 \text{ amps})^2 (9.0 \Omega) = .563 \text{ watts}$$

$$R_2 \rightarrow P = \frac{V^2}{R} = \frac{(2.3 \text{ V})^2}{(6.0 \Omega)} = .882 \text{ watts}$$

\* Voltage for resistors in parallel is all same, and same as battery (2.3 V)